




LM1771 Evaluation Board

National Semiconductor
Application Note 1477
Jeff Kissinger
July 2006

Introduction

The LM1771 is an efficient buck switching controller capable of converting an input voltage between 2.8V to 5.5V into a regulated output voltage as low as 0.8V. The LM1771 utilizes a constant on-time control scheme which eliminates the need for external compensation components. The LM1771 features a precision enable pin to allow for easy sequencing and flexibility in setting the operating range of the power supply. Three timing options are available which translates to three possible frequency options for any given output voltage. Available in the small-sized LLP-6 package, the LM1771 allows for a complete power supply design to occupy very little board space without sacrificing efficiency.

The LM1771 Evaluation Board was designed with space critical applications in mind. The entire power supply occupies less than .86" X .76" on a two layer PCB, but is capable of delivering a maximum continuous load current of 2A. The output voltage is set at 2.5V, but can be easily varied by replacing one of the feedback resistors. The 2000ns timing option (LM1771U) is used to attain a 378kHz switching frequency. The input voltage is nominally 5V, but can be varied over the entire operating range of the LM1771 (2.8V to 5.5V) for testing purposes. At the full 2A load, the efficiency of the power supply is greater than 92%.

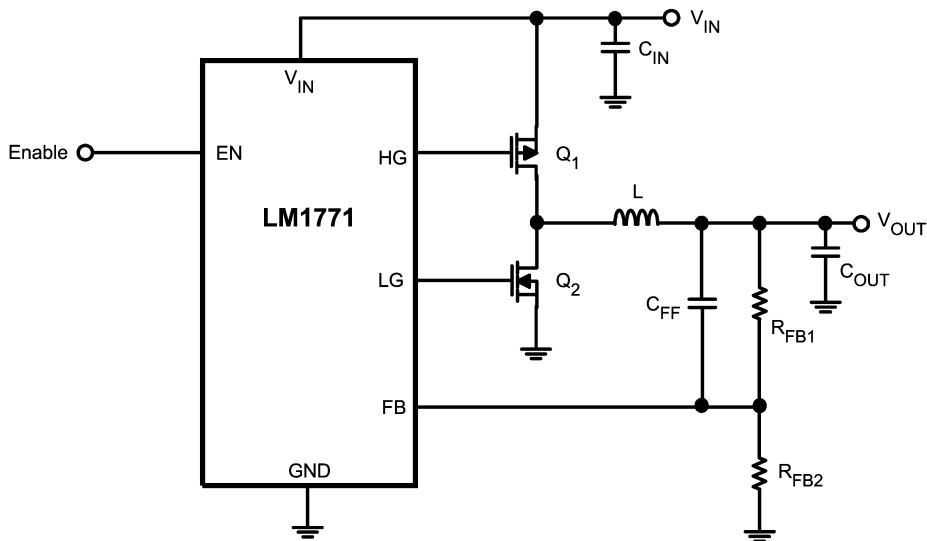


Schematic

20193301

Bill of Materials (5V to 2.5V Conversion)


Designator	Description	Part Number	Quantity	Manufacturer
U1	LM1771, 2000ns	LM1771USD/NOPB	1	National Semiconductor
Q1	PMOS	Si3867DV	1	Siliconix
Q2	NMOS	Si3460DV	1	Siliconix
Cin	22 μ F Capacitor, 0805	GRM21BR60J226ME39	1	Murata
Cout	68 μ F Capacitor, 6V, 55m Ω , C-Case	6TPC68M	1	Sanyo
Rfb1	21k Ω Resistor, 0603	CRCW06032102F	1	Vishay
Rfb2	10k Ω Resistor, 0603	CRCW06031002F	1	Vishay
L	5.0 μ H Inductor	MSS7341-502NLB	1	Coilcraft
Cff	1nF Capacitor, 0603	VJ0603102KXXA	1	Vishay
Test Points	Individual Test Points	160-1026-02-05-00	4	Wearnes

Performance

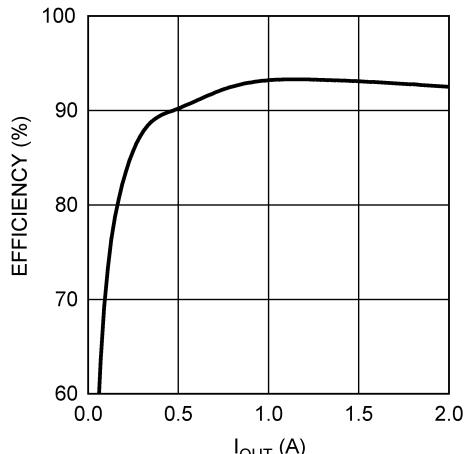Efficiency vs I_{OUT} ($V_{IN} = 5V$)

20193302


PCB Layout

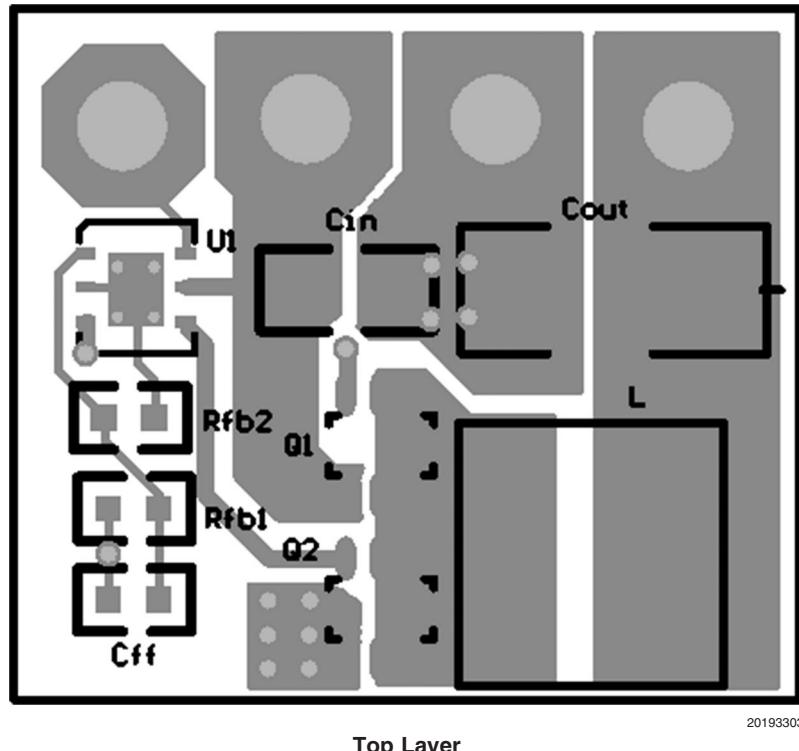

20193303

Top Layer

PCB Layout (Continued)

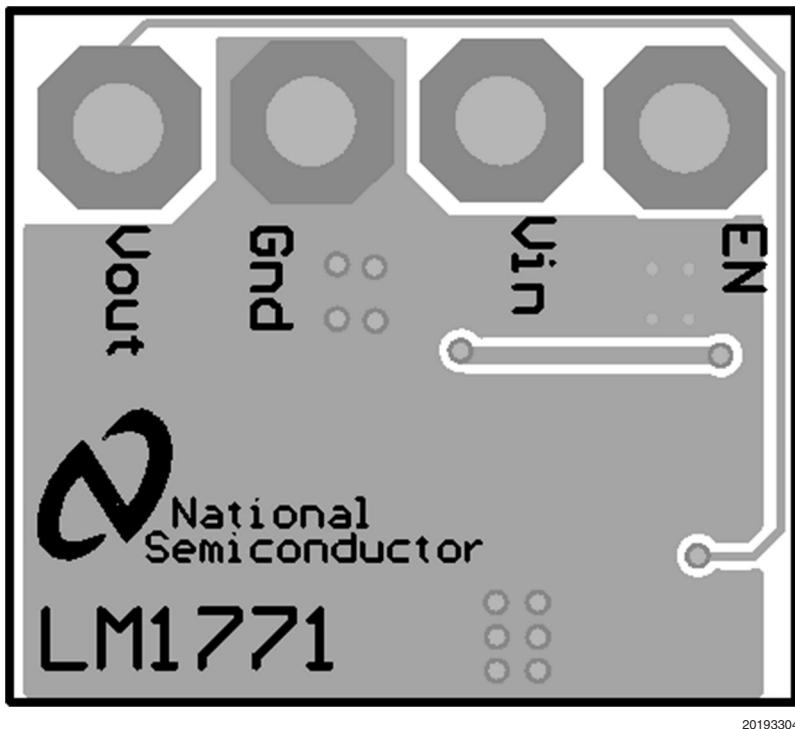

Bottom Layer

20193304

National does not assume any responsibility for use of any circuitry described, no circuit patent licenses are implied and National reserves the right at any time without notice to change said circuitry and specifications.

For the most current product information visit us at www.national.com.

LIFE SUPPORT POLICY

NATIONAL'S PRODUCTS ARE NOT AUTHORIZED FOR USE AS CRITICAL COMPONENTS IN LIFE SUPPORT DEVICES OR SYSTEMS WITHOUT THE EXPRESS WRITTEN APPROVAL OF THE PRESIDENT AND GENERAL COUNSEL OF NATIONAL SEMICONDUCTOR CORPORATION. As used herein:

1. Life support devices or systems are devices or systems which, (a) are intended for surgical implant into the body, or (b) support or sustain life, and whose failure to perform when properly used in accordance with instructions for use provided in the labeling, can be reasonably expected to result in a significant injury to the user.
2. A critical component is any component of a life support device or system whose failure to perform can be reasonably expected to cause the failure of the life support device or system, or to affect its safety or effectiveness.

BANNED SUBSTANCE COMPLIANCE

National Semiconductor follows the provisions of the Product Stewardship Guide for Customers (CSP-9-111C2) and Banned Substances and Materials of Interest Specification (CSP-9-111S2) for regulatory environmental compliance. Details may be found at: www.national.com/quality/green.

Lead free products are RoHS compliant.

 National Semiconductor
Americas Customer
Support Center
Email: new.feedback@nsc.com
Tel: 1-800-272-9959
www.national.com

National Semiconductor
Europe Customer Support Center
Fax: +49 (0) 180-530 85 86
Email: europe.support@nsc.com
Deutsch Tel: +49 (0) 69 9508 6208
English Tel: +44 (0) 870 24 0 2171
Français Tel: +33 (0) 1 41 91 8790

National Semiconductor
Asia Pacific Customer
Support Center
Email: ap.support@nsc.com

National Semiconductor
Japan Customer Support Center
Fax: 81-3-5639-7507
Email: jpn.feedback@nsc.com
Tel: 81-3-5639-7560