

LM3354/5 Evaluation Board

National Semiconductor
Application Note 1214
Clinton Jensen
October 2001



LM3354/5 Evaluation Board

Intoduction


The LM3354 and LM3355 are switched capacitor DC/DC converters which utilize a number of different gains to achieve output regulation. The LM3354/5 evaluation board is programmed for an output of 4.1V, ideal for White or Blue LED applications. An LM3354 1.8V option is also available.

The LM3355 is capable of up to 50mA of output current while the LM3354 is capable of up to 90mA of output current. See the LM3354 datasheet for more information on driving LED's or for information on other standard voltage options of the LM3354. A bill of materials and a schematic follow:

TABLE 1. LM3354/5 Evaluation Board List of Components

Designator	Description	Manufacturer
U1	LM3354/5 DC/DC Converter	National Semiconductor
C _{IN}	10µF ceramic capacitor (X5R, 6.3V)	Taiyo Yuden
C _{OUT}	10µF ceramic capacitor (X5R, 6.3V)	Taiyo Yuden
C1	0.33µF ceramic capacitor (X7R, 16V)	Taiyo Yuden
C2	0.33µF ceramic capacitor (X7R, 16V)	Taiyo Yuden
C _{FIL}	1µF ceramic capacitor (X7R, 10V)	Taiyo Yuden

Typical Application Circuit

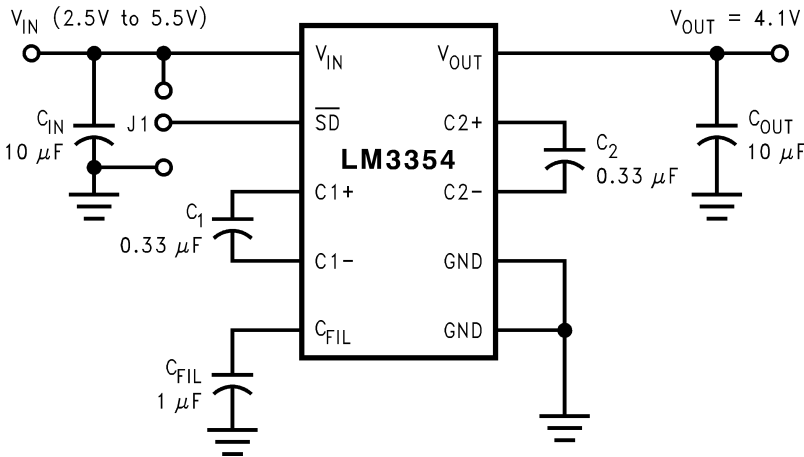


20028401

FIGURE 1. Basic Buck/Boost Regulator

AN-1214

Typical Application Circuit (Continued)

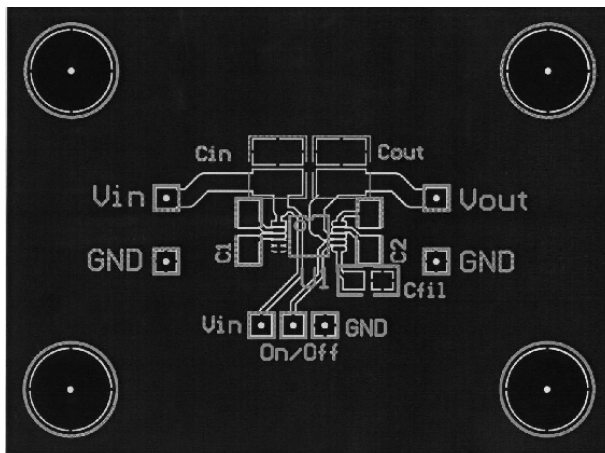

20028402

FIGURE 2. Typical Layout, Top View (magnification 1.5X)

LIFE SUPPORT POLICY

NATIONAL'S PRODUCTS ARE NOT AUTHORIZED FOR USE AS CRITICAL COMPONENTS IN LIFE SUPPORT DEVICES OR SYSTEMS WITHOUT THE EXPRESS WRITTEN APPROVAL OF THE PRESIDENT AND GENERAL COUNSEL OF NATIONAL SEMICONDUCTOR CORPORATION. As used herein:

1. Life support devices or systems are devices or systems which, (a) are intended for surgical implant into the body, or (b) support or sustain life, and whose failure to perform when properly used in accordance with instructions for use provided in the labeling, can be reasonably expected to result in a significant injury to the user.
2. A critical component is any component of a life support device or system whose failure to perform can be reasonably expected to cause the failure of the life support device or system, or to affect its safety or effectiveness.



National Semiconductor Corporation
Americas
Email: support@nsc.com

www.national.com

National Semiconductor Europe

Fax: +49 (0) 180-530 85 86
Email: europe.support@nsc.com
Deutsch Tel: +49 (0) 69 9508 6208
English Tel: +44 (0) 870 24 0 2171
Français Tel: +33 (0) 1 41 91 8790

National Semiconductor Asia Pacific Customer Response Group

Tel: 65-2544466
Fax: 65-2504466
Email: ap.support@nsc.com

National Semiconductor Japan Ltd.

Tel: 81-3-5639-7560
Fax: 81-3-5639-7507